

# Use the LM158/LM258/ LM358 Dual, Single Supply Op Amp

National Semiconductor  
Application Note 116  
August 1980



Use the LM158/LM258/LM358 Dual, Single Supply Op Amp

## INTRODUCTION

Use the LM158/LM258/LM358 dual op amp with a single supply in place of the LM1458/LM1558 with split supply and reap the profits in terms of:

- Input and output voltage range down to the negative (ground) rail
- Single supply operation
- Lower standby power dissipation
- Higher output voltage swing
- Lower input offset current
- Generally similar performance otherwise

The main advantage, of course, is that you can eliminate the negative supply in many applications and still retain equivalent op amp performance. Additionally, and in some cases more importantly, the input and output levels are permitted to swing down to ground (negative rail) potential. Table I shows the relative performance of the two in terms of guaranteed and/or typical specifications.

In many applications the LM158/LM258/LM358 can also be used directly in place of LM1558 for split supply operation.

## SINGLE SUPPLY OPERATION

The LM1458/LM1558 or similar op amps exhibit several important limitations when operated from a single positive (or negative) supply. Chief among these is that input and output signal swing is severely limited for a given supply as shown in Figure 1. For linear operation, the input voltage must not reach within 3 volts of ground or of the supply, and output range is similarly limited to within 3–5 volts of ground or supply. This means that operation with a +12V supply could be limited as low as 2 Vp-p output swing. The LM358 however, allows a 10.5 Vp-p output swing for the same 12V supply. Admittedly these are worst case specification limits, but they serve to illustrate the problem.

TABLE I. Comparison of Dual Op Amps LM1458 and LM358


Characteristic	LM1458	LM358
$V_{IO}$	6 mV Max	7 mV Max
CM $V_I$	24 Vp-p*	0–28.5V*
$I_{IO}$	200 nA	50 nA
$I_{OB}$	500 nA	–500 nA
CMRR	60 dB Min @ 100 Hz 90 dB Typ	85 dB Typ @ DC
$\bar{e}_n$ @ 1 kHz, $R_{GEN}$ 10 k $\Omega$	45 nV/ $\sqrt{Hz}$ Typ	40 nV/ $\sqrt{Hz}$ Typ**
$Z_{IN}$	200 M $\Omega$ Typ	Typ 100 M $\Omega$
$A_{VOL}$	20k Min 100k Typ	100k Typ
$f_c$	1.1 MHz Typ	1 MHz Typ**
$P_{BW}$	14 kHz Typ	11 kHz Typ**
$dV_O/dt$	0.8V/ $\mu$ s Typ	0.5V/ $\mu$ s Typ**
$V_O$ @ $R_L = 10k/2k$	24/20 Vp-p*	28.5 Vp-p
$I_{SC}$	20 mA Typ	Source 20 mA Min (40 Typ) Sink 10 mA Min (20 Typ)
PSRR @ DC	37 dB Min 90 dB Typ	100 dB Typ
$I_D$ ( $R_L = \infty$ )	8 mA Max	2 mA Max

‡From laboratory measurement


\*Based on  $V_S = 30V$  on LM358 only, or  $V_S = \pm 15V$

\*\*From data sheet typical curves

AN-116

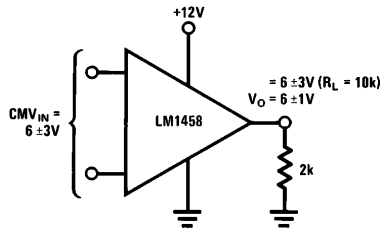


TL/H/7424-1

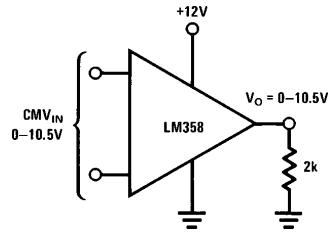


TL/H/7424-2

FIGURE 1. Worst Case Signal Levels with +12V Supply

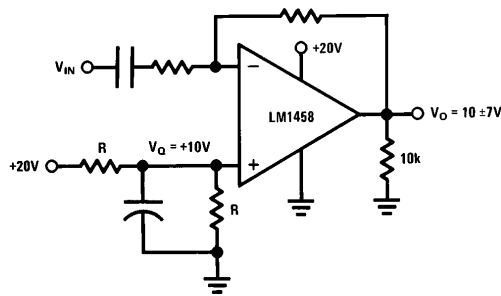

TL/H/7424-3

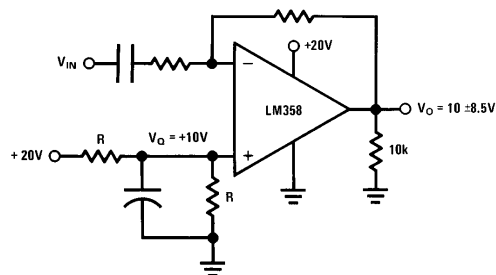

TL/H/7424-4

FIGURE 2. Operating with AC Signals

#### AC GAIN

For AC signals the input can be capacitor coupled. The input common mode and quiescent output voltages are fixed at one-half the supply voltage by a resistive divider at the non-inverting input as shown in Figure 2. This quiescent output could be set at a lower voltage to minimize power dissipation in the LM358, if desired, so long as  $V_Q \geq V_{IN}$  pk. For the LM1458 the quiescent output must be higher,  $V_Q \geq 3V + V_{IN}$  pk thus, for small signals, power dissipation is much greater with the LM1458. Example: Required  $V_O = V_Q \pm 1V$  pk into 2k,  $V_{SUPPLY} =$  as required. Find quiescent dissipation in load and amplifier for LM1458 and LM358.

LM358	LM1458
$V_Q = +1V$	$V_Q = 4V$
$V_{SUPPLY} = +3.5V$	$V_{SUPPLY} = 8V$
$P_{LOAD} = \frac{E_L^2}{R_L} = \frac{1}{2k} = 0.5 \text{ mW}$	$P_{LOAD} = \frac{4^2}{2k} = 8 \text{ mW}$
$P_D = V_{SL} I_S^* + (V_S - V_Q) I_L$	$P_D = P_D^* + (V_S - V_Q) I_L$
$= 3.5V \times 0.7 \text{ mA} + (3.5 - 1) \frac{1V}{2k}$	$= 22 \text{ mW} + (8 - 4) \frac{4V}{2k}$
$P_D = 2.45 + 1.25 = 3.7 \text{ mW}$	$P_D = 22 + 8 = 30 \text{ mW}$
$P_{TOTAL} = 3.7 + 0.5 = 4.2 \text{ mW}$	$P_{TOTAL} = 30 + 8 = 38 \text{ mW}$

\*From typical characteristics

\*From typical characteristics

The LM1458 requires over twice the supply voltage and nearly 10 times the supply power of the LM358 in this application.

#### INVERTING DC GAIN

Connections and biasing for DC inverting gain are essentially the same as for the AC coupled case. Note, of course, that the output cannot swing negative when operated from a single positive supply. Figure 3 shows the connections and signal limitations.


#### NON-INVERTING DC GAIN

The non-inverting gain connection does not require the  $V_Q$  biasing as before; the inverting input can be returned to ground in the usual manner for gains greater than unity, (see Figure 4). A tremendous advantage of the LM358 in this connection is that input signals and output may extend all the way to ground; therefore DC signals in the low-millivolt range can be handled. The LM1458 still requires that  $V_{IN} = 3-17V$ . Therefore maximum gain is limited to  $A_V = (V_O - 3)/3$ , or  $A_V \text{ max} = 5.4$  for a 20V supply.

There is no similar limitation for the LM358.
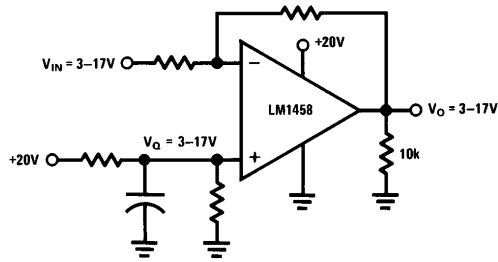
### ZERO T.C. INPUT BIAS CURRENT


An interesting and unusual characteristic is that  $I_{IN}$  has a zero temperature coefficient. This means that matched resistance is not required at the input, allowing omission of one resistor per op amp from the circuit in most cases.



TL/H/7424-5

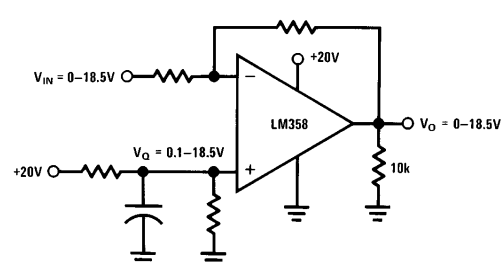
### BALANCED SUPPLY OPERATION

The LM358 will operate satisfactorily in balanced supply operation so long as a load is maintained from output to the negative supply.




TL/H/7424-6

FIGURE 3. Typical DC Coupled Inverting Gain

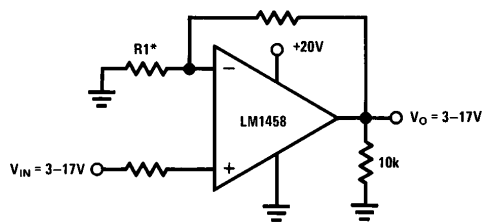

\* $R1 = \infty$  for  $A_V = +1$   
 $A_V \leq 5.4$  for 20V Supply


TL/H/7424-7

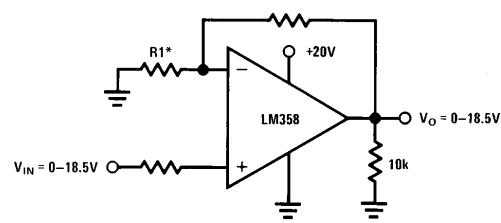

\* $R1 = \infty$  for  $A_V = +1$   
 $A_V$  not limited

TL/H/7424-8

FIGURE 4. Typical DC Coupled Non-Inverting Gain

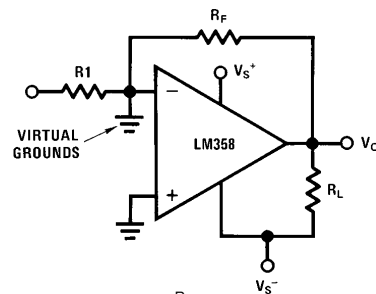

Crossover (distortion) occurs at  $V_O = V_{S-} \frac{R_F}{R_L + R_F}$

TL/H/7424-9

FIGURE 5. Split Supply Operation of LM358

The output load to negative supply forces the amplifier to source some minimum current at all times, thus eliminating crossover distortion. Crossover distortion without this load would be more severe than that expected with the normal op amp. Since the single supply design took notice of this normal load connection to ground, a class AB output stage was not included. Where ground referenced feedback resistors are used as in *Figure 5*, the required load to the negative supply depends upon the peak negative output signal level desired without exhibiting crossover distortion.  $R_L$  to the negative rail should be chosen small enough that the voltage divider formed by  $R_F$  and  $R_L$  will permit  $V_O$  to swing negative to the desired point according to the equation:

$$R_L = R_F \frac{V_S - V_O}{V_O}$$

$R_L$  could also be returned to the positive supply with the advantage that  $V_O$  max would never exceed  $(V_S^+ - 1.5V)$ . Then with  $\pm 15V$  supplies  $R_{L\ MIN}$  would be  $0.12 R_F$ . The disadvantage would be that the LM358 can source twice as much current as it can sink, therefore  $R_L$  to negative supply can be one-half the value of  $R_L$  to positive supply.

The need for single or split supply is based on system requirements which may be other than op amp oriented. However if the only need for balanced supplies is to simplify the biasing of op amps, there are many systems which can find a cost effective benefit in operating LM358's from single supplies rather than standard op amps from balanced supplies. Of the usual op amp circuits, Table II shows those few which have limited function with single supply operation. Most are based on the premise that to operate from a single supply, a reference  $V_Q$  at about one-half the supply be available for bias or (zero) signal reference. The basic circuits are those listed in AN-20.

**TABLE II. Conventional Op Amp Circuits Suitable for Single Supply Operation**

Application	Limitations
AC Coupled amp‡	$V_Q^*$
Inverting amp	$V_Q$
Non-inverting amp	OK*
Unity gain buffer	OK
Summing amp	$V_Q$
Difference amp	$V_Q$
Differentiator	$V_Q$
Integrator	$V_Q$
LP Filter	$V_Q$
I-V Connector	$V_Q$
PE Cell Amp	OK
I Source	$I_{O\ MIN} = \frac{1.5}{R_1}$
I sink	OK
Volt Ref	OK
FW Rectifier	$V_Q$ or modified circuit
Sine wave osc	$V_Q$
Triangle generator	$V_Q$
Threshold detector	OK
Tracking, regulator PS	Not practical
Programmable PS	OK
Peak Detector	OK to $V_{IN} = 0$

‡See AN20 for conventional circuits

\* $V_Q$  denotes need for a reference voltage, usually at about  $\frac{V_S}{2}$

OK means no reference voltage required

#### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

**National Semiconductor Europe**  
Fax: (+49) 0-180-530 85 86  
Email: chjwge tevm2.nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Français Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
13th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408